

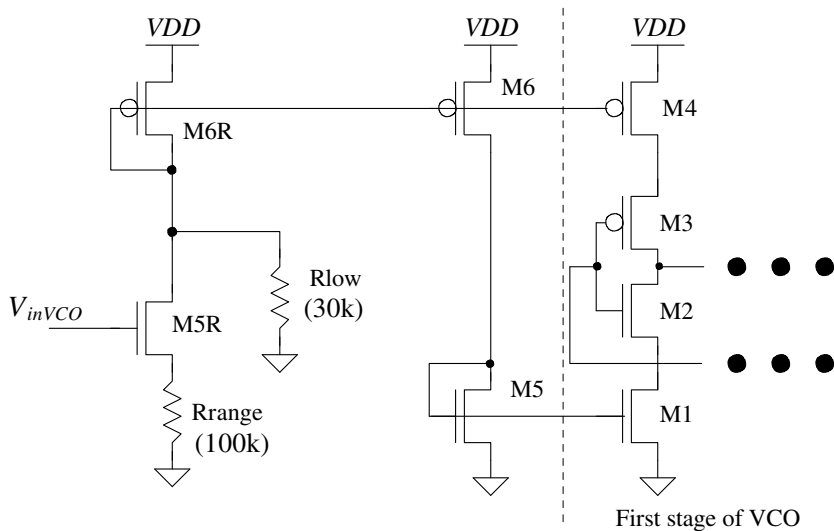


Figure 19.25 Limiting the current in a current-starved VCO.